

## LC3b Architecture

### Data Path

The data path includes the following major blocks:

1. Memory
2. Register File
3. ALU, PSR(flags) and sign/zero extenders
4. Program Counter

The interconnections of these blocks and corresponding control signals are shown in the figure:

#### **Description:**

##### **Memory:**

Memory consists of 256 byte space. Each byte is comprised of 8 bits. The 8 bits are divided into two 4-bit bytes, memH and memL for upper 4 and lower 4 bits respectively.




It has a latch I to select the address from PC/R6/AluOut. The address then decides which memory location is accessed. Control bits addr[0] and ctrl decide if memH or memL or both are active. It thus decides if we will access a word (8 bits) or a byte (4 bits).


When memWr is enabled, if we are writing a word, data is written from regH and regL into memH and memL respectively. Else, if we are writing a byte, data is written from regL into memH or memL depending upon which one of them is active.

When memRd is enabled, data is read from the corresponding memory location to either ir or mdr depending upon which bit is enabled among ir\_wr, mdr\_h, mdr\_l. If ir\_wr is enabled, complete 8 bit data is read from memory to ir register. If one of mdr\_h or mdr\_l is enabled, byte is read from one of memH or memL register into mdr[7:0] or mdr[3:0]. If both mdr\_h and mdr\_l are enabled, complete 8 bits word is read from memory to mdr[7:0].

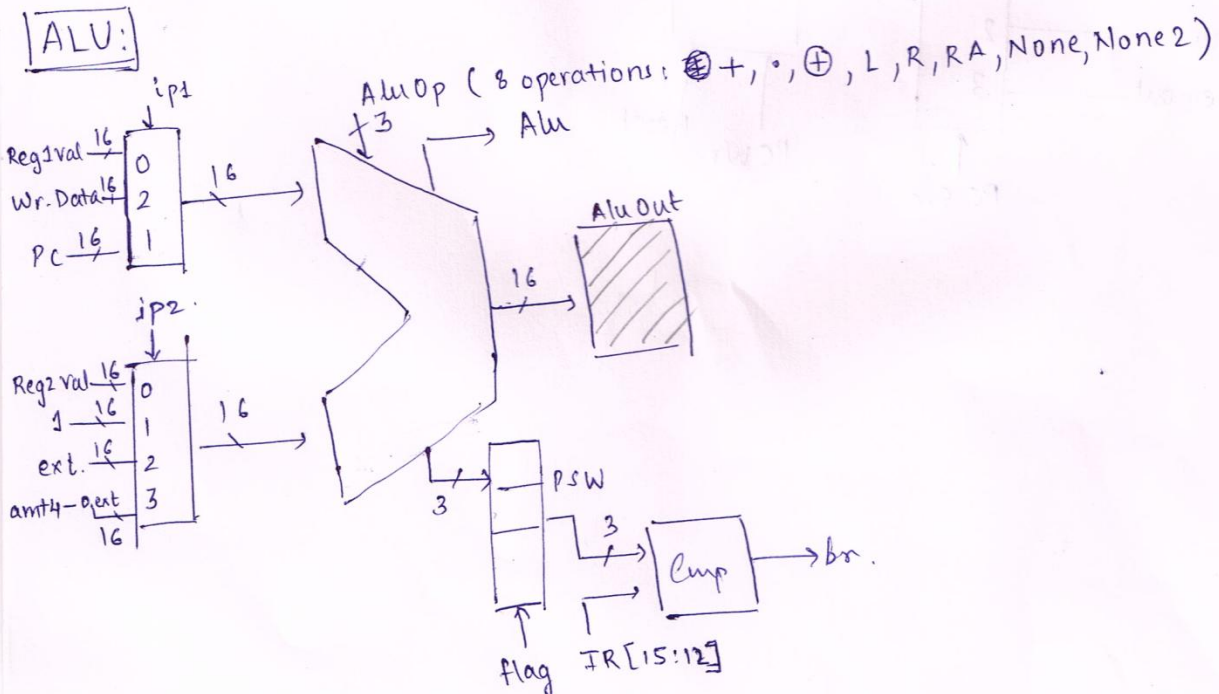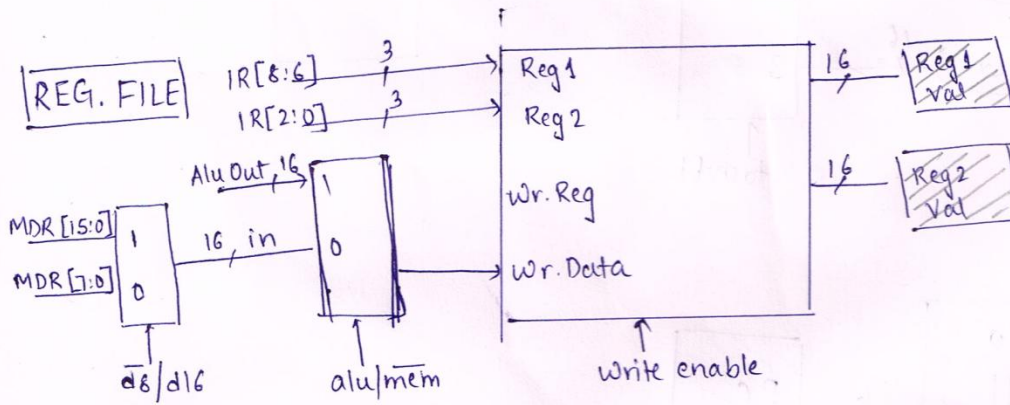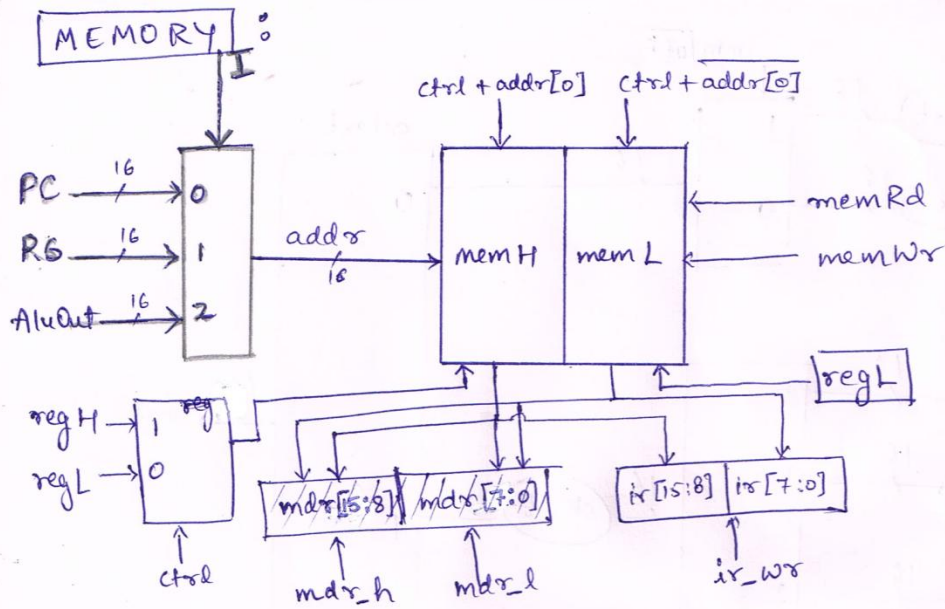
##### **Register File:**

Register file consists of 8 16 bit registers, 2 multiplexers with control bits d8\_d16 and alu\_mem which select whether to process 8 bit data or 16 bit data and whether to take data from memory or from alu respectively. Reg1val and Reg2val are two latches which implements reading function from registers according to the value given in IR. The control bit write\_en enables writing or loading a value into a particular register the address of which is given as input.



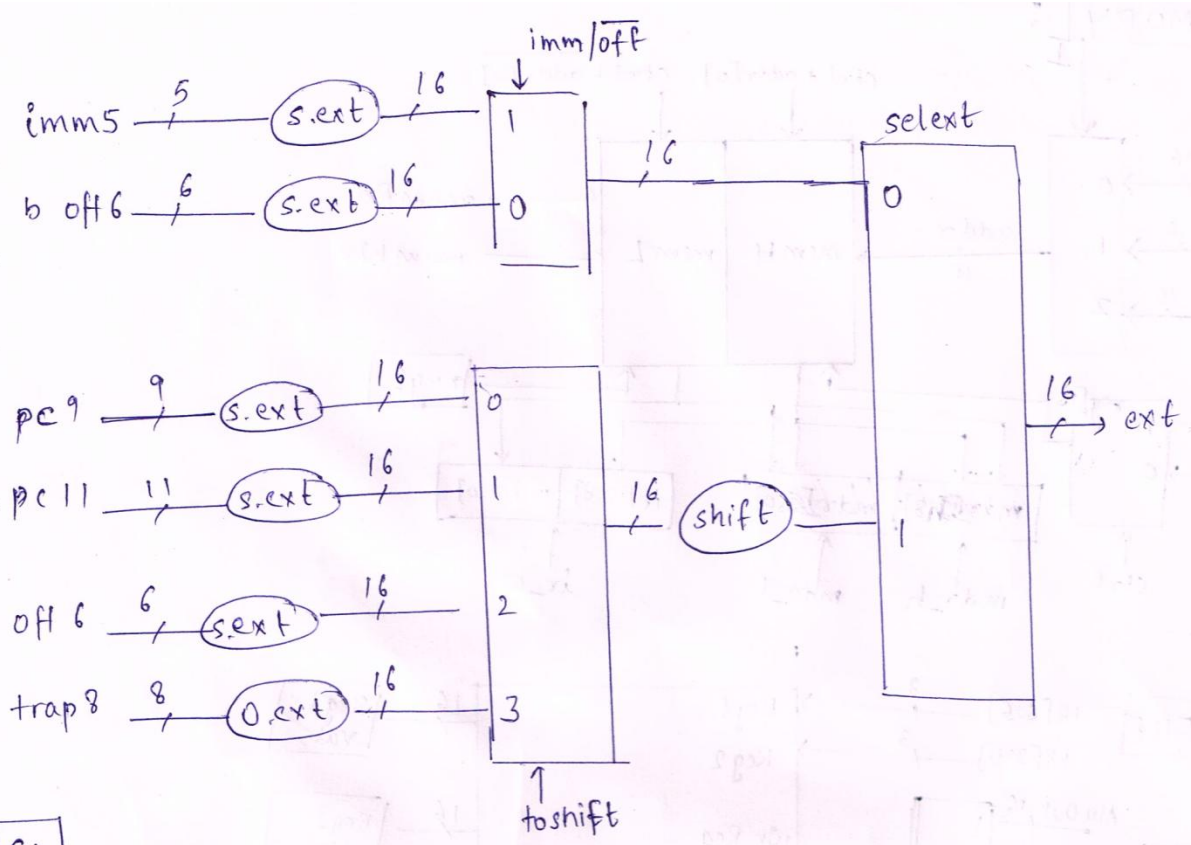

PC:

 

### **ALU:**

ALU performs 8 different operations, controlled by op: Add, And, XOR, Left shift, Right Shift, Right Shift Arithmetic, None1, None2. None operations give output=input. ALU has 2 inputs. None1 makes output=input1 and None2 makes output=input2.

Input 1 is selected from Reg1val, WrData(also a Regfile inputs, 8/16 bit version of MDR), PC, R6 by using a mux controlled by ip1 signal.

Input 2 is selected from Reg2val, 0x02, extender output, zero-extended amount4 by using a mux controlled by ip2 signal.

Extender unit has imm5, boff6, pc9, pc11, off6, trap8 as inputs. These are directly taken from corresponding instructions. Of these imm5, boff6 need only sign extension and pc9, pc11, off6, trap8 need sign/zero extension with left shift. These are controlled by 3 muxes controlled by: imm/off, toshift, sel\_ext.

Since alu is combinatorial, its output is also available in the same cycle. This output is called alu(wire). Output of ALU is stored in alu\_out latch for further use in other clock cycles.

ALU also controls flags. Flags get updated only when flag signal is set. Flags can be loaded by validating alu\_out latch or can be directly from memory(MDR). This is controlled by frm\_mem signal.

### **Program Counter:**

Program counter consists of a 16-bit register called pc(latch) and a mux with control line pc\_src. Input to the muxes are either Alu out or Alu or Mem out or 0x280h(in case of Interrupts). The value of the register pc gets updated with either of the inputs depending on the pc\_src value. Control bit pc\_wr enable writing to pc.

### **Note:**

- Same Memory block is used for both instructions and data( **Von Neumann architecture**).
- Clock and reset are external to both data and control path.
- All reset pins of individual blocks have the same name. This is because they are all tied together.

### **Control Path**


The control path has the following types of states like most RISC architectures:

1. Fetch
2. Decode
3. Execute
4. Memory Access
5. Write Back

Upon reset, reset pins of all the data path blocks are pulled high and the controller enters "Fetch" state in next clock cycle. It issues the corresponding control signals and jumps to next state at positive clock edge and this continues.

The reset operation clears register files, sets PC to start of memory and memory is loaded with the predefined Assembly Language code and corresponding data in specific memory locations.

The control flow is shown in the figure

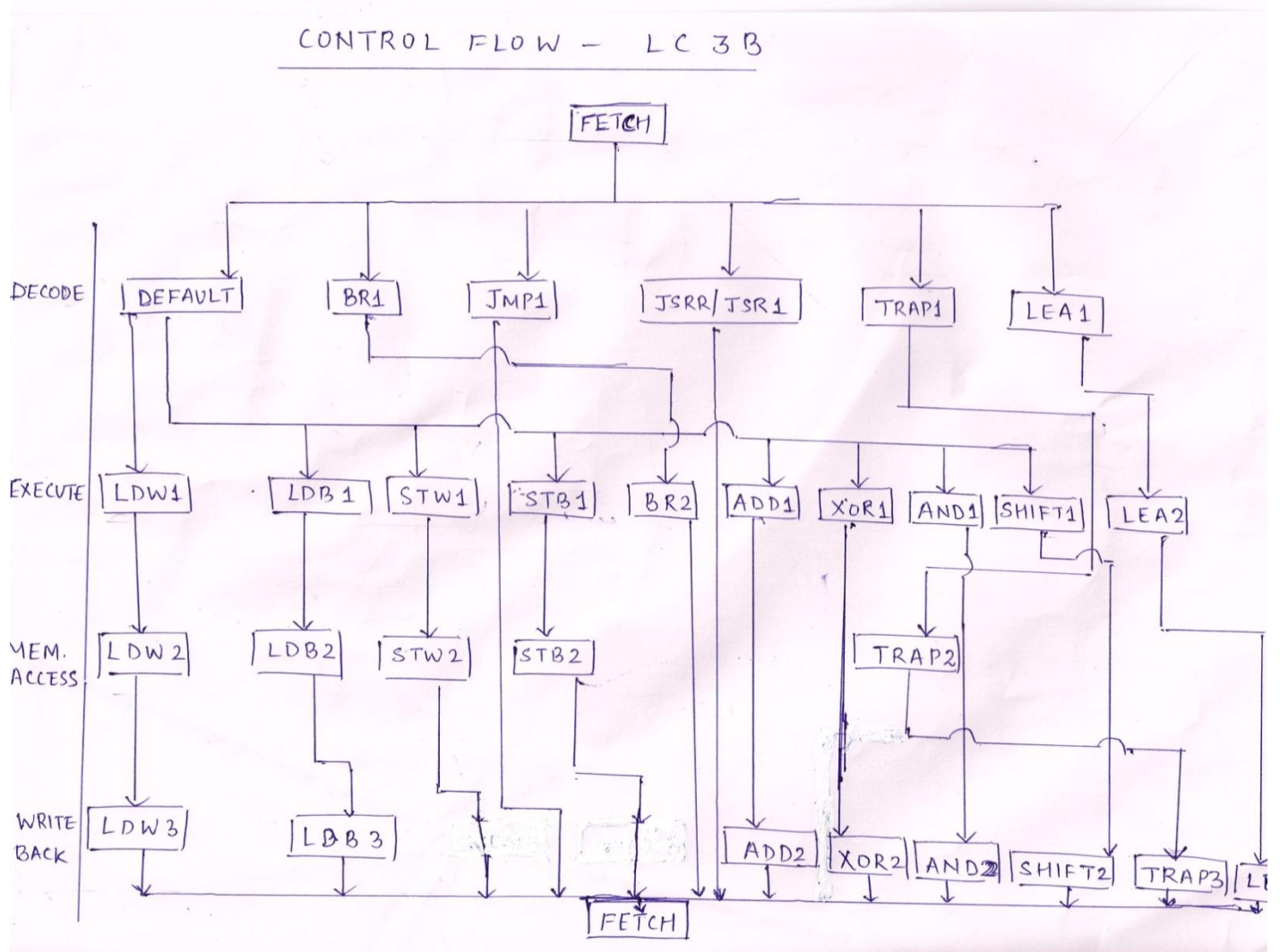

Control signals corresponding to each state are explained below:

## Fetch

1. Fetch:

Signals to enable memory read and disable write. Read line is selected to load address from PC. The instruction is written into IR(Instruction Register).

RegFile is disabled.

PC is loaded with PC+2 from ALU.

pc_src=2'b01; //from alu(imm) pc_wr=1'b1;	write_en=1'b0; reg_reset =1'b0;	l=0; memRd=1;
--	------------------------------------	------------------

pc_reset=1'b0;	ip1_sel=2'b01; ip2_sel=2'b01; op=3'b000; flag=0; frm_mem=0;	memWr=0; ctrl=1; ir_wr=1'b1; mdr_l=1'b0; mdr_h=1'b0; reset =0;
----------------	---	---

## Decode

### 2. Default:

Read Register1, Register 2 from Register File.

Disable all other blocks and corresponding latches read/write.

pc_wr=0; pc_reset=0;	write_en=0;  frm_mem=0; flag=0;	memRd=0; memWr=0; ir_wr=0; mdr_h=0; mdr_l=0;
-------------------------	--	--

### 3. BR1:

ALU adds shifted/sign extended pc-offset to pc. Output stays in alu\_out latch. Rest all is disabled.

pc_wr=0; pc_reset=0; ip2_sel=2'b10; write_en=0;	op = 3'b000; frm_mem=0; flag=0; toshift=2'b00; sel_ext=1; ip1_sel=2'b01;	memRd=0; memWr=0; ir_wr=0; mdr_h=0; mdr_l=0;
--	---	--

### 4. JMP1:

Register file reads BaseR into Reg1val latch. ALU passes Reg1val latch to PC. PC gets updated from alu in the same cycle.

pc_wr=0; pc_src=2'b01; pc_reset=0;	op = 3'b110; frm_mem=0; flag=0;	memRd=0; memWr=0; ir_wr=0;
--	---------------------------------------	----------------------------------

	imm_offb=0; sel_ext=0; ip1_sel=2'b00; ip2_sel=2'b10;	mdr_h=0; mdr_l=0;  write_en=0;
--	---	---

## 5. JSR(R)1:

Write R7 of regfile with PC by selecting appropriate read select line.

In case of JSRR, pass BaseR from Reg1val to PC.

In case of JSR, add left-shifted, sign-extended PCoffset to PC.

The result is written from alu to PC in the same cycle.

JSRR:

op = 3'b000; frm_mem=0; flag=0; imm_offb=0; sel_ext=0; ip1_sel=2'b00;        I ip2_sel=2'b10;	write_en=1; d8_d16=1; reg_reset=0; alu_mem=1; dr=3'b111;	memRd=0; memWr=0;  pc_wr=1; pc_src=2'b10; pc_reset=0;
---	--	--

JSR:

op = 3'b000; frm_mem=0; flag=0; toshift=1; sel_ext=1; ip1_sel=2'b01;	write_en=1; d8_d16=1; reg_reset=0; alu_mem=1; dr=3'b111; ip2_sel=2'b10;	memRd=0; memWr=0;  pc_wr=1; pc_src=2'b10; pc_reset=0;
---	--	--

## 6. TRAP1:

Write R7 of Regfile with PC value.

ALU calculates trap vector address by zero extending and left shifting the trap vector bits. It involves only one operand. Hence, ALU performs None-2 operation.

pc_wr=1; pc_src=2'b10; pc_reset=0;	op=3'b111; frm_mem=0; flag=0; toshift=2'd3; sel_ext=1;	memRd=0; memWr=0;  write_en=1; d8_d16=1;
--	--	--

	ip2_sel=2'd2;	reg_reset=0; alu_mem=1; dr=3'b111;
--	---------------	--

#### 7. LEA1:

ALU performs PC + left-shifted, sign-extended PCOffset. Rest all disabled.

sel_ext=1; ip1_sel=2'b01; ip2_sel=2'b10;  pc_wr=0; pc_reset=0;	write_en=0;  op = 3'b000; frm_mem=0; flag=1; toshift=2'b00;	memRd=0; memWr=0; ir_wr=0; mdr_h=0; mdr_l=0;
---	--	--

#### Execute

#### 8. LDW1:

Memory address is calculated in ALU. Rest all disabled.

pc_wr=0; pc_reset=0; op=3'b000; toshift=2'b10; sel_ext=1;	write_en=0;  ip1_sel=0; flag=0; ip2_sel=2'b10;	memRd=0; memWr=0; ir_wr=0; mdr_h=0; mdr_l=0;
---	--	--

#### 9. LDB1:

Memory address is calculated in ALU. Rest all disabled.

pc_wr=0; pc_reset=0;	ip1_sel=0; ip2_sel=2'b10; imm_offb=0; sel_ext=0; flag=0; op=3'b000;	memRd=0; memWr=0; ir_wr=0; mdr_h=0; mdr_l=0; write_en=0;
-------------------------	--	---

#### 10. STW1:



Memory address is calculated in ALU. Rest all disabled.

pc_wr=0; pc_reset=0;	write_en=0;  ip1_sel=0; flag=0; ip2_sel=2'b10; op=3'b000; toshift=2'b10; sel_ext=1;	memRd=0; memWr=0; ir_wr=0; mdr_h=0; mdr_l=0;
-------------------------	--	--

#### 11. STB1:

Memory address is calculated in ALU. Rest all disabled.

pc_wr=0; pc_reset=0;	ip1_sel=0; ip2_sel=2'b10; imm_offb=0; sel_ext=0;t flag=0; op=3'b000;	memRd=0; memWr=0; ir_wr=0; mdr_h=0; mdr_l=0;  write_en=0;
-------------------------	---	---

#### 12. BR2:

If branch is taken, load PC from alu\_out latch, else do nothing. Rest all disabled.

If branch taken:

pc_src=0; pc_wr=1;	write_en=0;  flag=0; frm_mem=0;	memRd=0; memWr=0; ir_wr=0; mdr_h=0; mdr_l=0;
-----------------------	--	--

If branch not taken:

pc_wr=0; pc_reset=0;	write_en=0;  flag=0; frm_mem=0;	memRd=0; memWr=0; ir_wr=0; mdr_h=0; mdr_l=0;
-------------------------	--	--

### 13. ADD1:

It selects 16 bit register value and adds it to the other 16 bit register value. Memory, PC write, register file and memory access are disabled.

ip1_sel=0; ip2_sel=0; op=3'b000;	pc_wr=0; pc_reset=0;  flag=0; frm_mem=0;	memRd=0; memWr=0; ir_wr=0; mdr_h=0; mdr_l=0;  write_en=0;
--	--	---

### 14. XOR1:

It selects 16 bit register value and xors it to the other 16 bit register value. Memory, PC write, register file and memory access are disabled.

ip1_sel=0; ip2_sel=0; op=3'b010;	pc_wr=0; pc_reset=0;  flag=0; frm_mem=0;	memRd=0; memWr=0; ir_wr=0; mdr_h=0; mdr_l=0;  write_en=0
--	--	--

### 15. AND1:

It selects 16 bit register value and xors it to the other 16 bit register value. Memory, PC write, register file and memory access are disabled.

ip1_sel=0; ip2_sel=0; op=3'b001;	pc_wr=0; pc_reset=0;  flag=0; frm_mem=0;	memRd=0; memWr=0; ir_wr=0; mdr_h=0; mdr_l=0;  write_en=0
--	--	--

### 16. SHIFT1:

It selects 16 bit register value and either shifts it either left or right or right arithmetic according to ir[5:4].Memory,PC write,register file and memory access are disabled.

if(ir[5:4]==2'b01) op=3'b100;  if(ir[5:4]==2'b10) op=3'b101;	flag=0; frm_mem=0;  ip1_sel=0; ip2_sel=0;  if(ir[5:4]==0) op=3'b011;	memRd=0; memWr=0; ir_wr=0; mdr_h=0; mdr_l=0; write_en=0 pc_wr=0; pc_reset=0;
--	---	---

#### 17. LEA2:

It selects 9 bit sign extended PCOffset value, left shifts it by 1 and add to PC latch value. Rest all disabled.

ip1_sel=1; ip2_sel=2'b10; op=3'b111; ip2_sel=2'd3; op=3'b100; op=3'b000;	write_en=0;  pc_wr=0; pc_reset=0;	memRd=0; memWr=0;  ir_wr=0; mdr_h=0; mdr_l=0;
---	--	--

### Memory Access

#### 18. LDW2:

It takes AluOut as address and reads word from that memory location into mdr\_h and mdr\_l. Rest all disabled.

flag=1'b0; frm_mem=1'b0;	write_en=1'b0;  pc_wr=1'b0; mdr_l=1'b1; mdr_h=1'b1; ir_wr=1'b0;	l=2'b10; memRd=1'b1; memWr=1'b0; ctrl=1'b1;
-----------------------------	--	--

#### 19. LDB2:

It takes AluOut as address and reads byte from that memory location into mdr\_l. Rest all disabled.

flag=1'b0;	write_en=1'b0;	l=2'b10;
------------	----------------	----------

frm_mem=1'b0; mdr_l=1'b1; mdr_h=1'b0; ir_wr=1'b0;	pc_wr=1'b0;	memRd=1'b1; memWr=1'b0; ctrl=1'b0;
--	-------------	--

#### 20. STW2:

It takes AluOut as address and writes word in that memory location from regL and regH. Rest all disabled.

flag=1'b0; frm_mem=1'b0;	write_en=1'b0;  pc_wr=1'b0; mdr_h=1'b0; ir_wr=1'b0;	l=2'b10; memRd=1'b0; memWr=1'b1; ctrl=1'b1; mdr_l=1'b0;
-----------------------------	---	---

#### 21. STB2:

It takes AluOut as address and writes byte in that memory location from regL. Rest all disabled.

flag=1'b0; frm_mem=1'b0; mdr_h=1'b0; ir_wr=1'b0;	write_en=1'b0;  pc_wr=1'b0; ctrl=1'b0;	l=2'b10; memRd=1'b0; memWr=1'b1; mdr_l=1'b0;
---	---	---

#### 22. TRAP2:

It takes AluOut as address and reads from that memory location to mdr\_l and mdr\_h. Rest all disabled.

ctrl=1'b1; mdr_l=1'b1; mdr_h=1'b1; ir_wr=1'b0;	write_en=1'b0;  pc_wr=1'b0;	l=2'b10; memRd=1'b1; memWr=1'b0; flag=1'b0; frm_mem=1'b0;
---	-----------------------------------	---

### Write Back

#### 23. LDW3:

16-bit mdr is written into wrdata and then Right arithmetic performed over it. Rest all disabled.

ip1_sel=2'd2; op=3'd6;	pc_wr=0; pc_reset=0;	memRd=0; memWr=0;
---------------------------	-------------------------	----------------------

frm_mem=0; flag=1;	reg_reset=0; d8_d16=1; alu_mem=0; dr=ir[11:9];	ir_wr=0; mdr_h=0; mdr_l=0;  write_en=1;
-----------------------	---	---

#### 24. LDB3:

8-bit mdr is written into wrdata and then taken into ALU without any operation. Rest all disabled.

ip1_sel=2'd2; op=3'd7; frm_mem=0; flag=1; pc_wr=0; pc_reset=0;	reg_reset=0; d8_d16=0; alu_mem=0; dr=ir[11:9];  write_en=1;	memRd=0; memWr=0; ir_wr=0; mdr_h=0; mdr_l=0;
---	--	--

#### 25. ALU2 (ADD2 / XOR2 / AND2 / SHIFT2):

AluOut is written into wrdata and then taken into ALU without any operation. Rest all disabled.

ip1_sel=2'd2; op=3'd7; frm_mem=0; flag=1;	reg_reset=0; alu_mem=1; dr=ir[11:9];  pc_wr=0; pc_reset=0;	memRd=0; memWr=0; ir_wr=0; mdr_h=0; mdr_l=0; write_en=1;
--	---	---

#### 26. TRAP3:

It writes from memout to PC. Rest all are disabled.

pc_wr=1; pc_reset=0; pc_src=2'd3;	write_en=0;  frm_mem=0; flag=0;	memRd=0; memWr=0; ir_wr=0; mdr_h=0; mdr_l=0;
---	--	--

#### 27. LEA3:

16-bit mdr is written into wrdata and then taken into ALU with no operation. Rest all disabled.

ip1_sel=2'd2; op=3'd7;  frm_mem=0; flag=1;	reg_reset=0; d8_d16=1; alu_mem=0; dr=ir[11:9];  pc_wr=0; pc_reset=0;	memRd=0; memWr=0; ir_wr=0; mdr_h=0; mdr_l=0;  write_en=1;
--	--	---

### Control States followed by different instructions

Write Back	Memory Access	Execute	Decode	Fetch	Instruction
ALU2		ADD1	Default	Fetch	ADD
ALU2		AND1	Default	Fetch	AND
		BR2	BR1	Fetch	BR
			JMP1	Fetch	JMP
			JSR(R)1	Fetch	JSR(R)
LDB3	LDB2	LDB1	Default	Fetch	LDB
LDB3	LDB2	LDB1	Default	Fetch	LDW
LEA3		LEA2	LEA1	Fetch	LEA
SHIFT2		SHIFT1	Default	Fetch	SHF
	STB2	STB1	Default	Fetch	STB
	STW2	STW1	Default	Fetch	STW
TRAP3	TRAP2		TRAP1	Fetch	TRAP
XOR2		XOR1	Default	Fetch	XOR